

Birla Institute of Technology and Science Pilani
CS F342 Computer Architecture
Second Semester 2017-18
Test-2 (27th February 2018)


Duration: 35 minutes

Marks: 5 Marks

A BCD adder is to be designed to add two digit BCD numbers A and B . Assume that at any given time the input is a valid BCD number. The sum is a two digit BCD number S and a 1-bit carry $cout$.

Implement a BCD adder as per the following architecture.

 1. 4-bit adder should be implemented using a single assign statement.
2. BCD adjustment unit should be implemented using data flow modeling.



Implement the following using Verilog HDL. Provide a suitable test bench for the module.

Include the following cases in your test bench:

$A = 8'h\ 25$, $B = 8'h\ 52$

$A = 8'h\ 99$, $B = 8'h\ 88$

$A = 8'h\ 93$, $B = 8'h\ 12$

NOTE: When you submit the file make sure that you save it with the name

bcd_adder_your_first_name.v

Example: If your name is Rahul Saraswat, name the file as *bcd_adder_rahul.v* also include name and ID No. in the first two lines (comment these lines) of your code.

***** End of Paper*****